

CA HW3 B05901011 電機四 許秉倫

rtl_tb1

```
START!!! Simulation Start .....
```

```
=====  
Congratulations!!! Your answer is correct!
```

rtl_tb2

```
START!!! Simulation Start .....
```

```
=====  
Congratulations!!! Your answer is correct!
```

gatelevel_tb1

```
START!!! Simulation Start .....
```

```
-----  
SDF File ./matvecmult_syn.sdf were used for this simulation.  
=====
```

```
Congratulations!!! Your answer is correct!
```

gatelevel_tb2

```
START!!! Simulation Start .....
```

```
-----  
SDF File ./matvecmult_syn.sdf were used for this simulation.  
=====
```

```
Congratulations!!! Your answer is correct!
```

no latch

```
Inferred memory devices in process  
in routine matvecmult line 89 in file  
'/home/raid7_2/userb05/b05011/CA/hw3/matvecmult.v'.  
=====
```

Register Name	Type	Width	Bus	MB	AR	AS	SR	SS	ST
counter_r_reg	Flip-flop	8	Y	N	Y	N	N	N	N
y_r_reg	Flip-flop	128	Y	N	Y	N	N	N	N

```
=====
```

timing report

add_0_root_add_1_root_add_48_15/U1_2/CO (ADDFXL)	0.86	5.62 r
add_0_root_add_1_root_add_48_15/U1_3/S (ADDFXL)	0.62	6.24 r
add_0_root_add_1_root_add_48_15/SUM[3] (matvecmult_DW01_add_0)	0.00	6.24 r
add_0_root_add_48_15/B[3] (matvecmult_DW01_add_15)	0.00	6.24 r
add_0_root_add_48_15/U1_3/CO (ADDFXL)	0.86	7.10 r
add_0_root_add_48_15/U1_4/S (ADDFXL)	0.61	7.71 r
add_0_root_add_48_15/SUM[4] (matvecmult_DW01_add_15)	0.00	7.71 r
add_76/A_5_ (matvecmult_DW01_add_14)	0.00	7.71 r
add_76/U1_5/CO (ADDFXL)	0.80	8.51 r
add_76/U1_6/S (ADDFXL)	0.68	9.19 r
add_76/SUM_6_ (matvecmult_DW01_add_14)	0.00	9.19 r
U208/Y (INVX3)	0.45	9.64 f
U272/Y (OAI2BB2XL)	0.51	10.15 r
y_r_reg_0__6_/D (DFFRX2)	0.00	10.15 r
data arrival time		10.15
clock CLK (rise edge)	10.00	10.00
clock network delay (ideal)	0.50	10.50
clock uncertainty	-0.10	10.40
y_r_reg_0__6_/CK (DFFRX2)	0.00	10.40 r
library setup time	-0.22	10.18
data required time		10.18

data required time		10.18
data arrival time		-10.15

slack (MET)		0.03

area report


```
Library(s) Used:
    slow (File: /home/raid7_2/course/cvsg/CBDBK_I

Number of ports:          1207
Number of nets:           2972
Number of cells:          1651
Number of combinational cells: 1465
Number of sequential cells:  153
Number of macros/black boxes: 0
Number of buf/inv:        209
Number of references:      54

Combinational area:      18318.341019
Buf/Inv area:            841.910387
Noncombinational area:   5037.883209
Macro/Black Box area:    0.000000
Net Interconnect area:   186294.270599

Total cell area:         23356.224228
Total area:              209650.494828
1
```

design and difficulty

 

首先，將電路拆成Sequential和combinational的part。我設定兩個狀態，分別是Y和counter。

Sequential part: 負責在clock來的時候更新Y及counter。

Combinational part: 當一個cycle來的時候，吃入新的值，並把新的值經過運算得到next state，接著輸出output。

因為是第一次寫verilog所以整個概念還有語法都要從頭摸索，導致花了蠻多時間在這個作業上的，但寫完後覺得很有成就感！